

# 1P2H Digital Electronics 1 – Solutions

Mark Cannon

Trinity Term 2026

## 1. Switching circuits

In circuit (a), the lamp is lit if  $A = 1$  and  $(B = 1$  or  $C = 0)$ , i.e.

$$a.(b + \bar{c}) = f_a.$$

In circuit (b), the lamp is NOT lit if  $A = 0$  or  $(B = 0$  and  $C = 1)$ , i.e.

$$\bar{a} + \bar{b}.c = \bar{f}_b.$$

By De Morgan's law

$$\bar{f}_b = \bar{a} + \bar{b}.c = \overline{a.(b + \bar{c})} = \bar{f}_a \quad \iff \quad f_a = f_b.$$

## 2. Boolean algebra

(a).

$a$	$b$	$c$	$d$	$f$	$a$	$b$	$c$	$d$	$f$	$a$	$b$	$c$	$d$	$f$	$a$	$b$	$c$	$d$	$f$
0	0	0	0	1	0	1	0	0	0	1	0	0	0	1	1	1	0	0	1
0	0	0	1	0	0	1	0	1	0	1	0	0	1	0	1	1	0	1	1
0	0	1	0	1	0	1	1	0	0	1	0	1	0	1	1	1	1	0	1
0	0	1	1	1	0	1	1	1	1	1	0	1	1	1	1	1	1	1	1

(b). Reduced SOP form by algebra:

$$\begin{aligned}
 f &= ab(a\bar{c} + c\bar{d}) + cd + \bar{b}\bar{d} \\
 &= ab(\bar{c} + c\bar{d}) + cd + \bar{b}\bar{d} && \text{(since } a.a = a) \\
 &= ab(\bar{c} + \bar{d}) + cd + \bar{b}\bar{d} && \text{(race-hazard)} \\
 &= ab(\overline{cd}) + cd + \bar{b}\bar{d} && \text{(De Morgan)} \\
 &= ab + cd + \bar{b}\bar{d}. && \text{(race-hazard)}
 \end{aligned}$$

Canonical SOP form can be obtained from the truth table by selecting entries when  $f = 1$ . This gives 11 minterms.

Alternatively, we have 5 terms when  $f = 0$ :

$$\bar{f} = \bar{a}\bar{b}\bar{c}d + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}bc\bar{d} + \bar{a}b\bar{c}\bar{d}$$

Applying De Morgan's law twice gives

$$f = (a + b + c + \bar{d}).(a + \bar{b} + c + d).(a + \bar{b} + c + \bar{d}).(a + \bar{b} + \bar{c} + d).(\bar{a} + b + c + \bar{d})$$

- (c). Write out truth table and compare with table for  $f$  in part (a).  
If they are the same then equivalence proved.

### 3. Karnaugh maps

(a).

$a$	$b$	$c$	$a(b + \bar{c})$	$b\bar{c}$	$\bar{a}\bar{c}$	$f_1$
0	0	0	0	0	1	1
0	0	1	0	0	0	0
0	1	0	0	1	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	1
1	0	1	0	0	0	0
1	1	0	1	1	0	1
1	1	1	1	0	0	1



$a \backslash bc$	00	01	11	10
0	1	0	0	1
1	1	0	1	1

$f_1 = a.b + \bar{c}$

(b).

$a$	$b$	$c$	$d$	$\bar{a}b$	$\bar{a}\bar{b}\bar{d}$	$\bar{c}$	$\bar{a}cd$	$f_2$
0	0	0	0	0	1	1	0	1
0	0	0	1	0	0	1	0	1
0	0	1	0	0	1	0	0	1
0	0	1	1	0	0	0	1	1
0	1	0	0	1	0	1	0	1
0	1	0	1	1	0	1	0	1
0	1	1	0	1	0	0	0	1
0	1	1	1	1	0	0	1	1
1	0	0	0	0	0	1	0	1
1	0	0	1	0	0	1	0	1
1	0	1	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0
1	1	0	0	0	0	1	0	1
1	1	0	1	0	0	1	0	1
1	1	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0



$ab \backslash cd$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	0	0
10	1	1	0	0

$\bar{f}_2 = a.c$  or  $f_2 = \bar{a} + \bar{c}$

(c).

$a$	$b$	$c$	$d$	$(a \oplus b).(c \oplus d)$	$abc$	$\bar{a}\bar{b}\bar{c}\bar{d}$	$\bar{a}\bar{b}cd$	$f_3$
0	0	0	0	$0.0 = 0$	0	0	0	0
0	0	0	1	$0.1 = 0$	0	0	0	0
0	0	1	0	$0.1 = 0$	0	0	0	0
0	0	1	1	$0.0 = 0$	0	0	0	0
0	1	0	0	$1.0 = 0$	0	1	0	1
0	1	0	1	$1.1 = 1$	0	0	0	1
0	1	1	0	$1.1 = 1$	0	0	0	1
0	1	1	1	$1.0 = 0$	0	0	0	0
1	0	0	0	$1.0 = 0$	0	0	0	0
1	0	0	1	$1.1 = 1$	0	0	0	1
1	0	1	0	$1.1 = 1$	0	0	0	1
1	0	1	1	$1.0 = 0$	0	0	1	1
1	1	0	0	$0.0 = 0$	0	0	0	0
1	1	0	1	$0.1 = 0$	0	0	0	0
1	1	1	0	$0.1 = 0$	1	0	0	1
1	1	1	1	$0.0 = 0$	1	0	0	1

⇒

	$cd$	00	01	11	10
$ab$	00	0	0	0	0
	01	1	1	0	1
	11	0	0	1	1
	10	0	1	1	1

OR

	$cd$	00	01	11	10
$ab$	00	0	0	0	0
	01	1	1	0	1
	11	0	0	1	1
	10	0	1	1	1

$$f_3 = a.c + \bar{a}.b\bar{c} + a.\bar{b}.d + \bar{a}.b.\bar{d}$$

$$f_3 = a.c + \bar{a}.b\bar{c} + a.\bar{b}.d + b.c.\bar{d}$$

(d).

$a$	$b$	$c$	$d$	$ab$ or $d\bar{c}$	$\bar{b}\bar{d}$ or $\bar{a}\bar{d}\bar{c}$	$f_3$
0	0	0	0	0	1	0
0	0	0	1	1	0	1
0	0	1	0	0	1	0
0	0	1	1	0	0	X
0	1	0	0	0	1	0
0	1	0	1	1	0	1
0	1	1	0	0	0	X
0	1	1	1	0	0	X
1	0	0	0	0	1	0
1	0	0	1	1	0	1
1	0	1	0	0	1	0
1	0	1	1	0	0	X
1	1	0	0	1	0	1
1	1	0	1	1	0	1
1	1	1	0	1	0	1
1	1	1	1	1	0	1

$\Rightarrow$

$ab \backslash cd$	00	01	11	10
00	1	1	X	0
01	0	1	X	X
11	1	1	1	1
10	0	1	X	0

$\bar{f}_4 = a.c + d$

(e). The worst Karnaugh map is the one that doesn't allow any adjacent 1s to be amalgamated. This gives a checkerboard pattern:

$ab \backslash cd$	00	01	11	10
00	1	0	1	0
01	0	1	0	1
11	1	0	1	0
10	0	1	0	1

The negation of this function is just as bad. The corresponding Boolean function has the property that a change in the value of just one of the variables always changes the value of the result. The function is therefore often used as a parity check on the validity of the bits in a byte. This is the same property enjoyed by the exclusive-or function. The worst SOP Karnaugh map has the very neat expression:

$$a \oplus b \oplus c \oplus d$$

#### 4. MOSFET operation and CMOS


(a). Positive voltage on Gate draws electrons between Drain and Source to form a continuous  $n$ -region.

(b). The first stage on left provides  $\bar{b}$ .


Consider  $n$ -channel devices at bottom half of second stage. The output  $f$  will be at 0V if ( $\bar{b} = 5V$  or  $a = 5V$ ) and  $c = 5V$ . So

$$\bar{f} = (a + \bar{b}).c \quad \text{or} \quad f = \bar{a}.b + \bar{c}$$

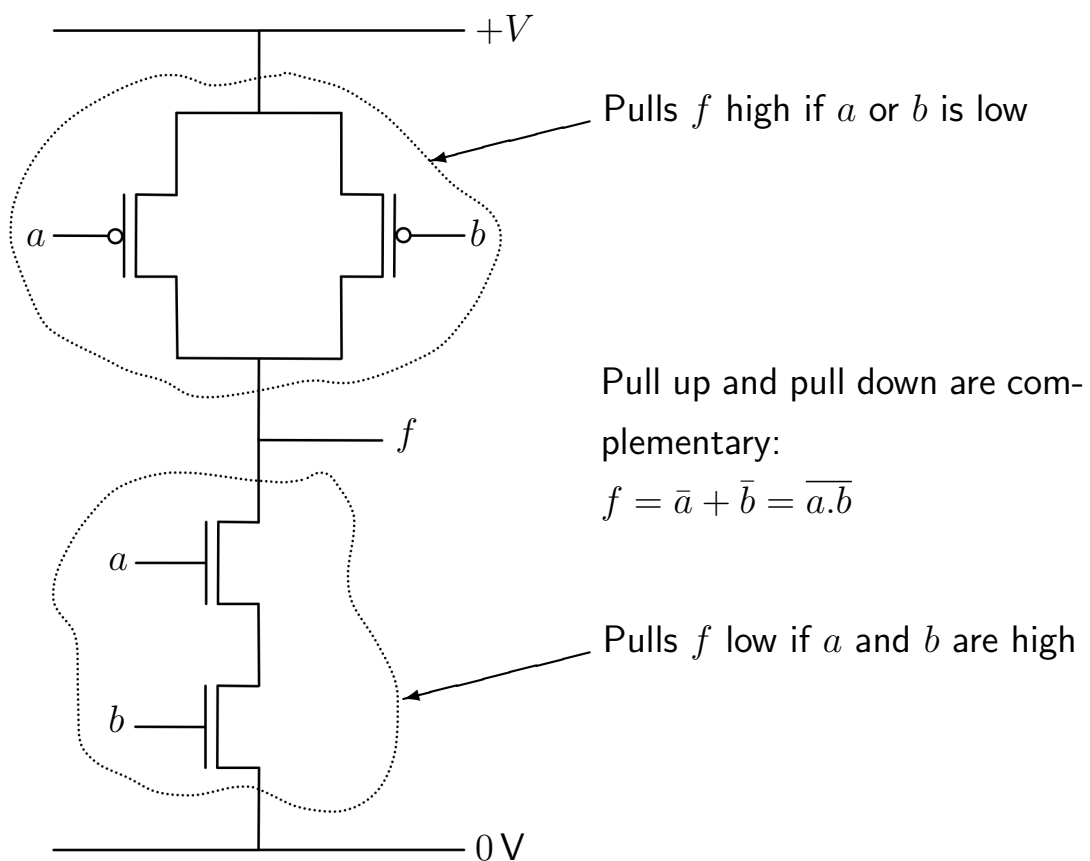(c).  $f = \bar{a}.b$  (NAND) – consider conditions on  $a$  and  $b$  for  $f = 0$  and  $f = 1$ :




 For  $g = a.b$  (AND), use  $\bar{g} = \overline{a.b}$ , i.e. NAND + NOT:



Note that if a FET is in parallel for the pull down side, then it must be in series on the pull up side.

 Note also that we CANNOT do this:  
because the n-channel devices won't work for pull up and p-channel devices can't pull down.




## 5. Binary codes

(a). Largest value =  $2^{16} - 1 = 65535$ , smallest = 0.

(b). Offset binary: largest =  $2^{16} - 1 - 2^{15} = 32767 = \text{FFFF}_{\text{Hex}}$   
 smallest =  $-2^{15} = -32768 = \text{0000}_{\text{Hex}}$

(c).  $-1 \rightarrow \text{FFFF}_{\text{Hex}}$

(d).

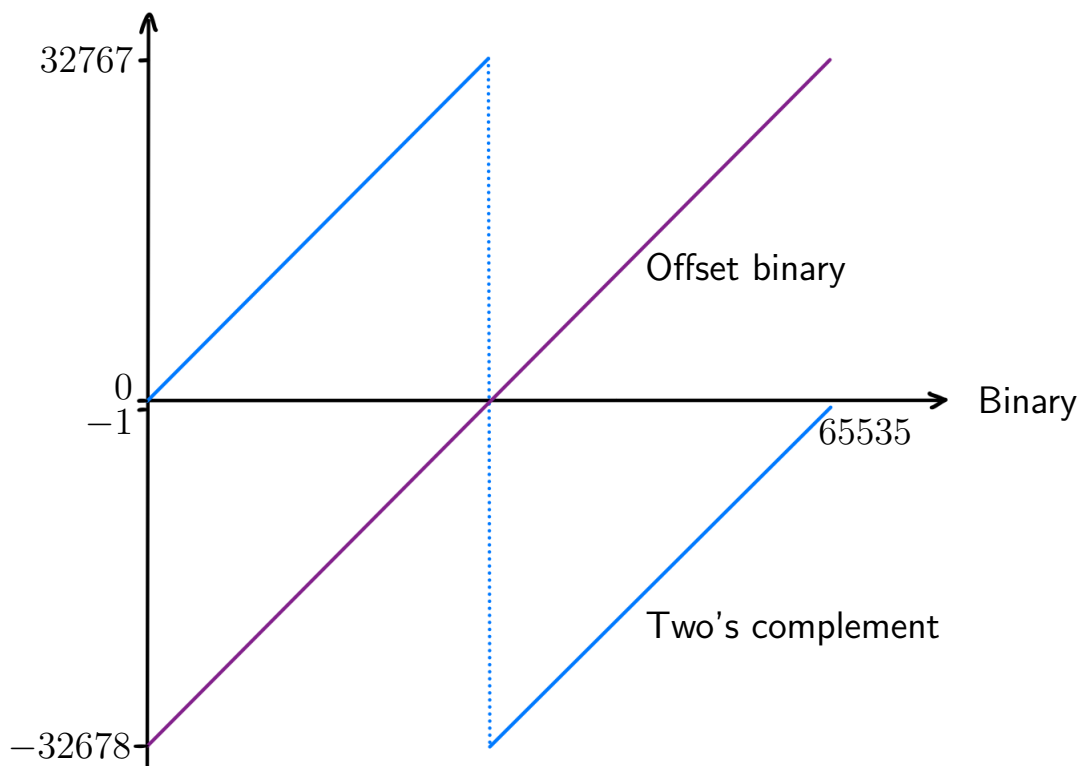

(e). BCD – Binary coded decimal, used for preserving the decimal representation of a number. Could be used, for example, to store telephone numbers in a directory.

Gray – unit distance code, only one bit changes between represented numbers. Often used when converting analogue to digital where bit changes arise from a physical process, i.e. an optical encoder.

(f). Gray code (reflected binary):



## 1P2H/9

$$\begin{array}{r} \text{then } 2^n + b = \quad 1 \quad 0 \quad 0 \quad 0 \quad \cdots \quad 0 \\ \quad \quad \quad + \quad 0 \quad b_{n-1} \quad b_{n-2} \quad b_{n-3} \quad \cdots \quad b_0 \\ \hline \quad \quad \quad 1 \quad b_{n-1} \quad b_{n-2} \quad b_{n-3} \quad \cdots \quad b_0 \end{array}$$

so the least significant  $n$  bits aren't affected by the addition.

(d).  $2^n + (b - c) = b - c$  in bit positions  $0 \rightarrow n - 1$

But  $2^n + (b - c) = (2^n - c) + b$  because of (c)

$2^n - c$  creates the 2's complement of  $c$ , and hence the 2's complement of  $c$  can be used with addition to compute  $b - c$ .

(e). Hex 03  $\rightarrow$  FD (2's complement)

$$\begin{array}{r} \text{So} \quad 40 \quad \text{is equivalent to} \quad 40 \quad \implies \quad 40_{\text{Hex}} - 03_{\text{Hex}} = 3D_{\text{Hex}} \\ \quad \quad \quad -03 \\ \hline \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad +FD \\ \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \hline \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad 13D \end{array}$$

## 7. Adders and subtractors

(a). Carry out is generated when the addition of two  $n$ -bit numbers is too large to fit into  $n$  bits.

$$C_{\text{out}} = 1 \text{ when } A_{n-1}A_{n-2} \cdots A_0 + B_{n-1}B_{n-2} \cdots B_0 \geq 2^n.$$

(b). Overflow is generated when the result is of incorrect sign and is therefore relevant to signed arithmetic only.

$$\begin{array}{l} \text{i.e. } +\text{ve} + +\text{ve} \rightarrow -\text{ve} \Rightarrow \text{overflow} \\ \quad \quad -\text{ve} + -\text{ve} \rightarrow +\text{ve} \Rightarrow \text{overflow} \end{array}$$

(c). Ripple adder – it takes time for the effect of the carries to “ripple” along the full-adder circuits.

Look-ahead carry – compute the carry using faster logic, which is helpful if a carry dependent decision is required.

## 8. Fixed point arithmetic

(a). Smallest number = 0000.0001 =  $1/16$

(b). Largest number = 1111.1111 =  $2^4 - 1/16 = 255/16$

(c). Yes, simple binary addition.

(d). Consider the multiplication of two fixed point numbers  $C = A \times B$

$A$  has the form  $A = a_i | a_f$ , where  $a_i =$  integer (4 bits)

$a_f =$  fraction (4 bits)

$$\implies A = a_i + a_f/2^4$$

$$\implies C = c_i + c_f/2^4 = a_i \times b_i + a_i \times b_f/2^4 + a_f \times b_f/2^8$$

Two potential problems:  $c_i > 2^4 - 1 \implies$  overflow

$c_f > 1 \implies$  underflow

(i) OK, (ii) underflow, (iii) overflow.

Possible algorithm:

1). Treat both numbers as 8-bit integers:  $A = \frac{1}{2^4}(2^4 \times a_i + a_f)$

2). Multiply the two 8-bit numbers to give

$$A \times B = \frac{1}{2^8} [(2^4 \times a_i + a_f) \times (2^4 \times b_i + b_f)] \text{ (16-bit result)}$$

3). Shift result right 4 places.

4). If rounding, then add the carry to the result of 3),

if truncating, discard carry.

5). If leading 8 bits are non-zero, then signal overflow,

else just discard the leading 8 bits in the 16-bit result,  
and return the least significant 8 bits.

## 9. Floating point number representation

$$\boxed{s \quad E + 63 \quad \text{mantissa, } f} \quad \Rightarrow \quad (-1)^s \times 2^E \times 1.f$$

Largest positive number is

$$\begin{aligned} & 0 \mid 111 \ 1110 \mid 1111 \ 1111 \\ &= 1 \times 2^{126-63} \times 1.1111 \ 1111 \\ &= 1 \times 2^{63} \times \left(2 - \frac{1}{256}\right) \\ &= 1.841 \times 10^{19} \end{aligned}$$